


EE 287 PROJECT NOTES

- a filter whose impulse response is of finite duration
- operate only on current and past input values
- provide a linear phase response
- always stable because they are implemented using an all zero transfer function

Project: Finite Impulse Response (FIR) Filter



Consists:

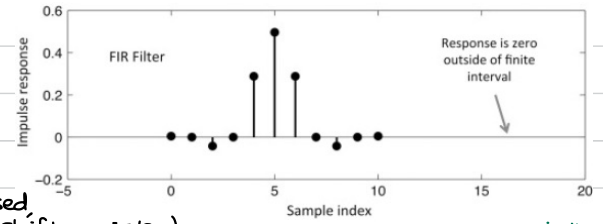- 29 samples
- multiply each by a constant
- sum together to get result
- Everything is signed
- First & last 14 coefficients are the same
- FIR contains last 29 samples for sampling
- when new samples are processed, the oldest are discarded (like shift register)




Requirements:

- Needs to run at 300 MHz
- Limited to 5 complex multipliers
- No more than 3 clock cycles per filter operation (100 MHz sample rate)
- Input FIFO w/ two flag push model
 - At least 4 samples
- Input data: fixed binary point 1.23 signed data (Range: $-1 < x < 1$)
- Coefficients: fixed signed binary point 3.24 (Range: $-4 < x < 4$)
- Output data: fixed binary point 8.24
 - Filter can have a gain > 1
 - Higher precision is kept internally
 - Results are rounded towards zero (truncate positive values, increment negative values in position 8.25)
 - All values reset to 0 (including FIFO)

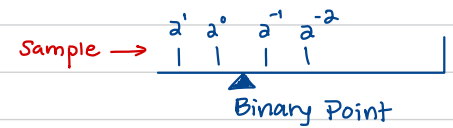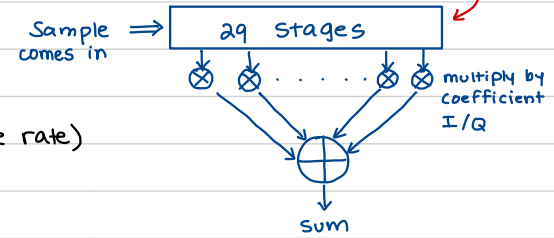

Notes:

- TB always takes data (flags)
- For bit size, add 5 bits extra above and below to both sides of binary point to avoid overflow
 - Adding 5 bits above/below will require summation to be 9.29 (38 bits)
- Use DesignWare for multipliers
- Capitalization matters (double check signals)
- Synthesis will take approx. 4-5 hours (big design)
- 5 complex multiplications each clock cycle
- I is Real and Q is Imaginary
- Data after a multiply of 3.24 and 1.24 is 4.47 format (only 8.24 will be in final answer)
- Will provide the prompt on CANVAS
- He will give TB this weekend (encrypted) for us to see how it works

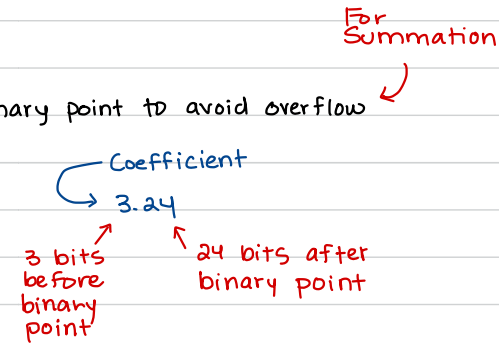

Note:

The design can be simplified if the first and last data are added, and then multiplied by the first coefficient. $28/2 \Rightarrow 14$ multiplies + 1 for center $\Rightarrow 15$ multiplies / 5 multiplies/clock $\Rightarrow 3$ clocks/filter result. (The test bench only sends coefficient 0-14, 0 and 28 are the same value)


- Project Steps:

- 29 samples where each sample is 48 bits (24 real and 24 imaginary)
- 1392 FFs (29 samples * 48 bits)
- 810 coefficients
- 2202 samples (1392 samples + 810 coefficients)

$$(A_I + A_Q) * (B_I + B_Q)$$

$$\begin{matrix} \text{Real} & \text{Imaginary} & \text{Imaginary} & \text{Real} \\ A_I B_I & A_I B_Q & A_Q B_I & - (A_Q B_Q) \end{matrix}$$
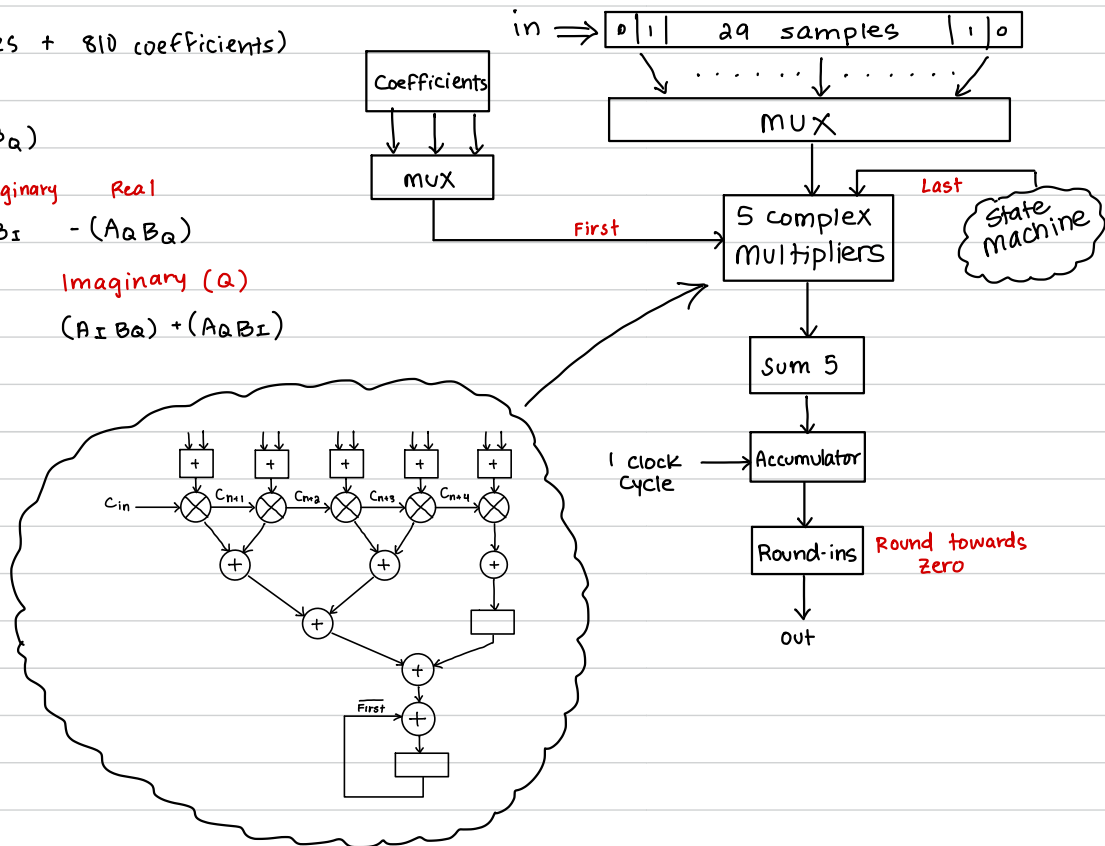
$$\begin{matrix} \text{Real (I)} & \text{Imaginary (Q)} \\ (A_I B_I) - (A_Q B_Q) & (A_I B_Q) + (A_Q B_I) \end{matrix}$$



Interface:

The design will consist of a single module named fir29. This module may include other modules as desired. The DW02_mult modules will be included in the test bench.

Name	Width	Dir	Comment
Clk	1	In	Rising edge clock
Reset	1	In	Active high reset signal
PushIn	1	In	A sample push signal
StopIn	1	Out	The input cannot accept a sample
SampI	24	In	The real part of the sample in 1.23 format
SampQ	24	In	The imaginary part of the sample in 1.23 format
PushCoef	1	In	Indicates loading a coefficient
CoefAddr	5	In	The coefficient location 0-15 valid
CoefI	27	In	The coefficient Real part 3.24 format
CoefQ	27	In	The coefficient Imaginary part 3.24 format
PushOut	1	Out	Data out of the filter.
FI	32	Out	Real filtered output 8.24 format
FQ	32	Out	Imaginary filtered output 8.24 format

TEAM MEETING NOTES/ TO DO :

4/12/23

- Share notes
- Create list of questions
- Create list of possible approaches
- Review together on Monday (4/17) @ 230 PM